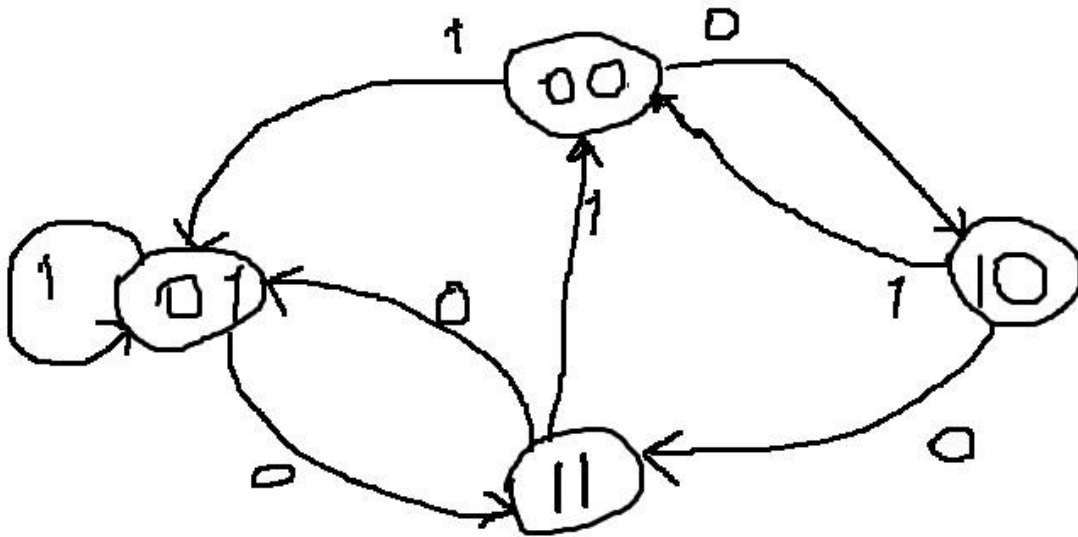


Assignment 4

1. Design a sequential circuit using T flipflops where the states change in the following way.



2. Design a 3bits synchronous down counter using SR FF.